

# **High-Speed Data Links in CMOS Technology**

**Ping Gui  
Jinghong Chen**

**Department of Electrical Engineering  
Southern Methodist University**

**Fermi Lab  
Oct. 05, 2010**

# Outline

- ◆ **The GigaBit Transceiver (GBT) Project with CERN**
  - A 5-Gbit/s Radiation-Tolerant Optical Receiver of the GBT Project for SLHC
  - A High-Resolution Phase Shifter (50-ps-Resolution and 25-ns Range) of the GBT Project for SLHC
  
- ◆ **Serializer and Laser Driver Design**
  
- ◆ **PLL Design**
  - Wideband LC Fractional-N PLL
  - Ring PLL
  
- ◆ **Summary**

# GigaBit Transceiver (GBT) Link Architecture


## Defined in the "DG White Paper"

### ◆ "Work Package 3-1"


- **Objective:**
  - ◆ Development of an high speed bidirectional radiation hard optical link, incorporating DAQ, TTC, and Slow Control into a single link.
- **Deliverable:**
  - ◆ Tested and qualified radiation hard optical link
- **Duration:**
  - ◆ 4 years (2008 – 2011)
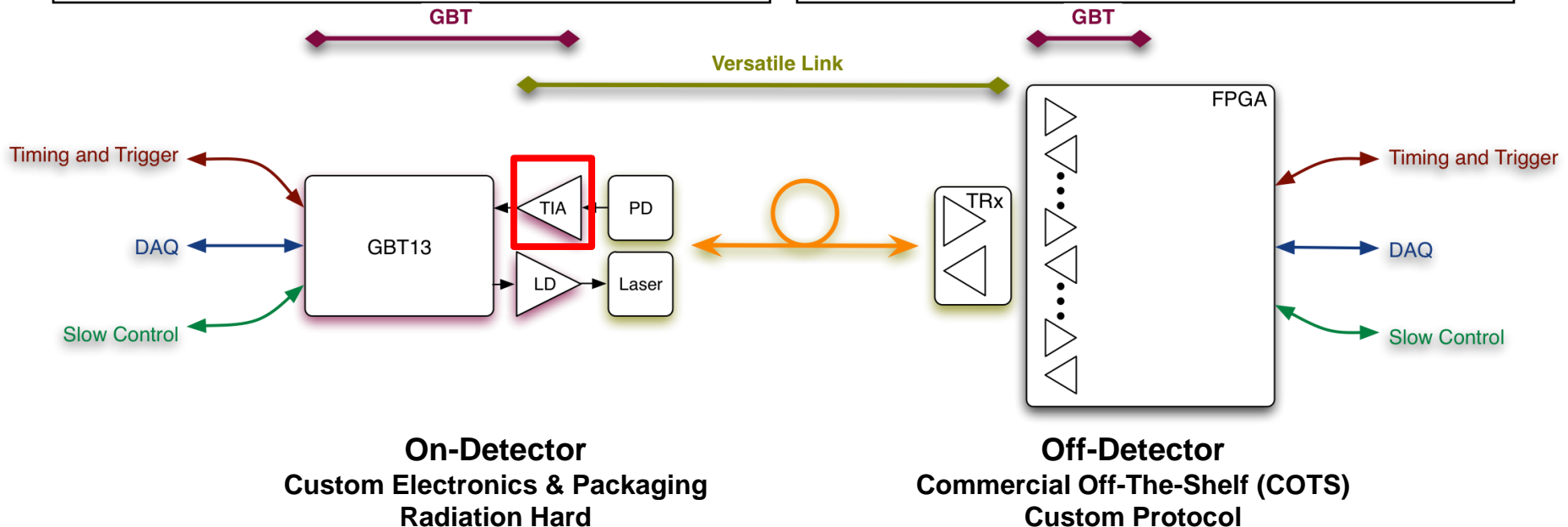
## Radiation Hard Optical Link:

- ◆ **GBT project: (led by Paulo Moreira)**
  - ASIC design
  - Verification
  - Functionality testing
  - Packaging
- ◆ **Versatile link project (led by Jan Troska)**
  - Opto-electronics
  - Radiation hardness
  - Functionality testing
  - Packaging




# GBT-SERDES

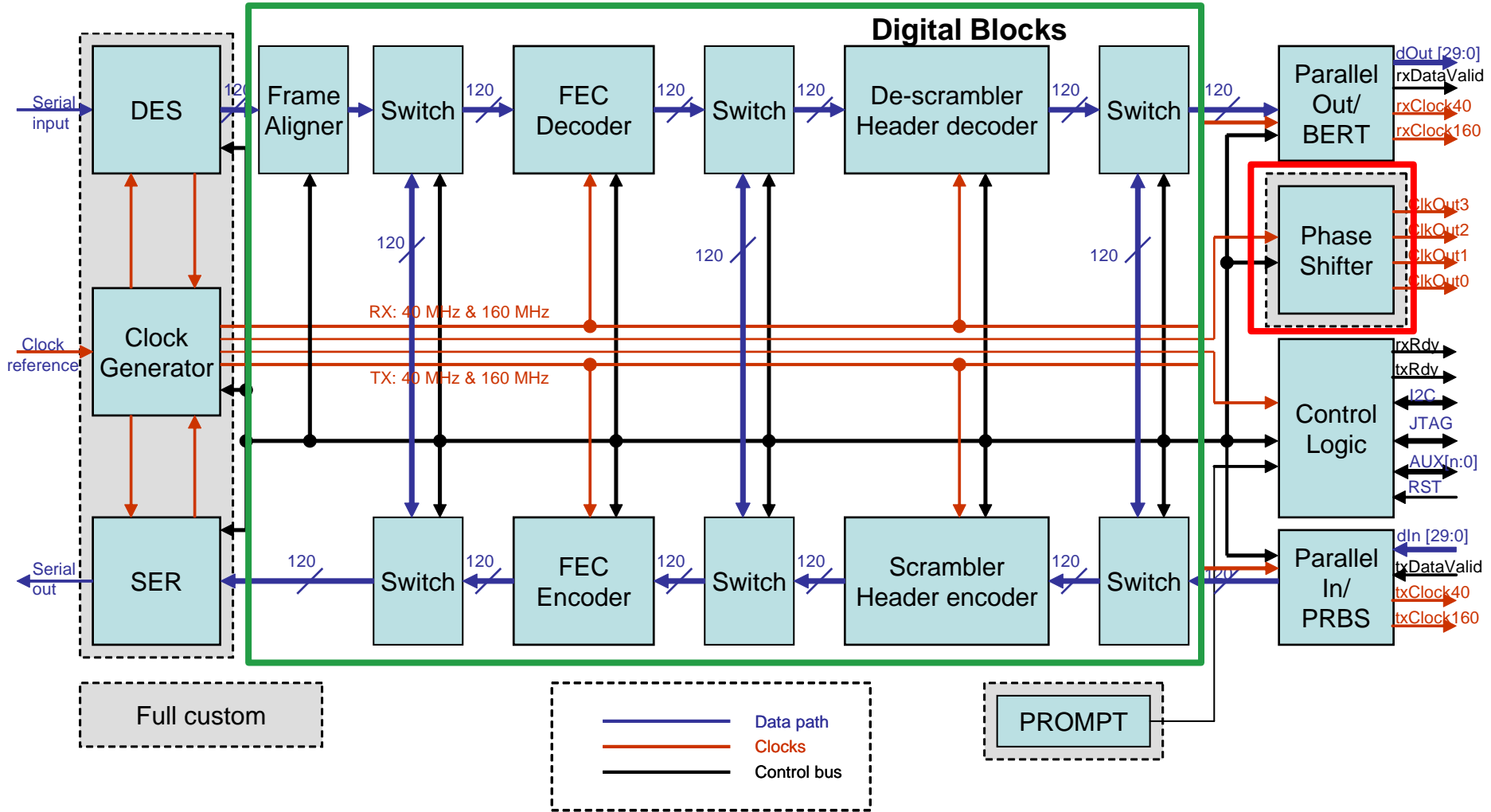
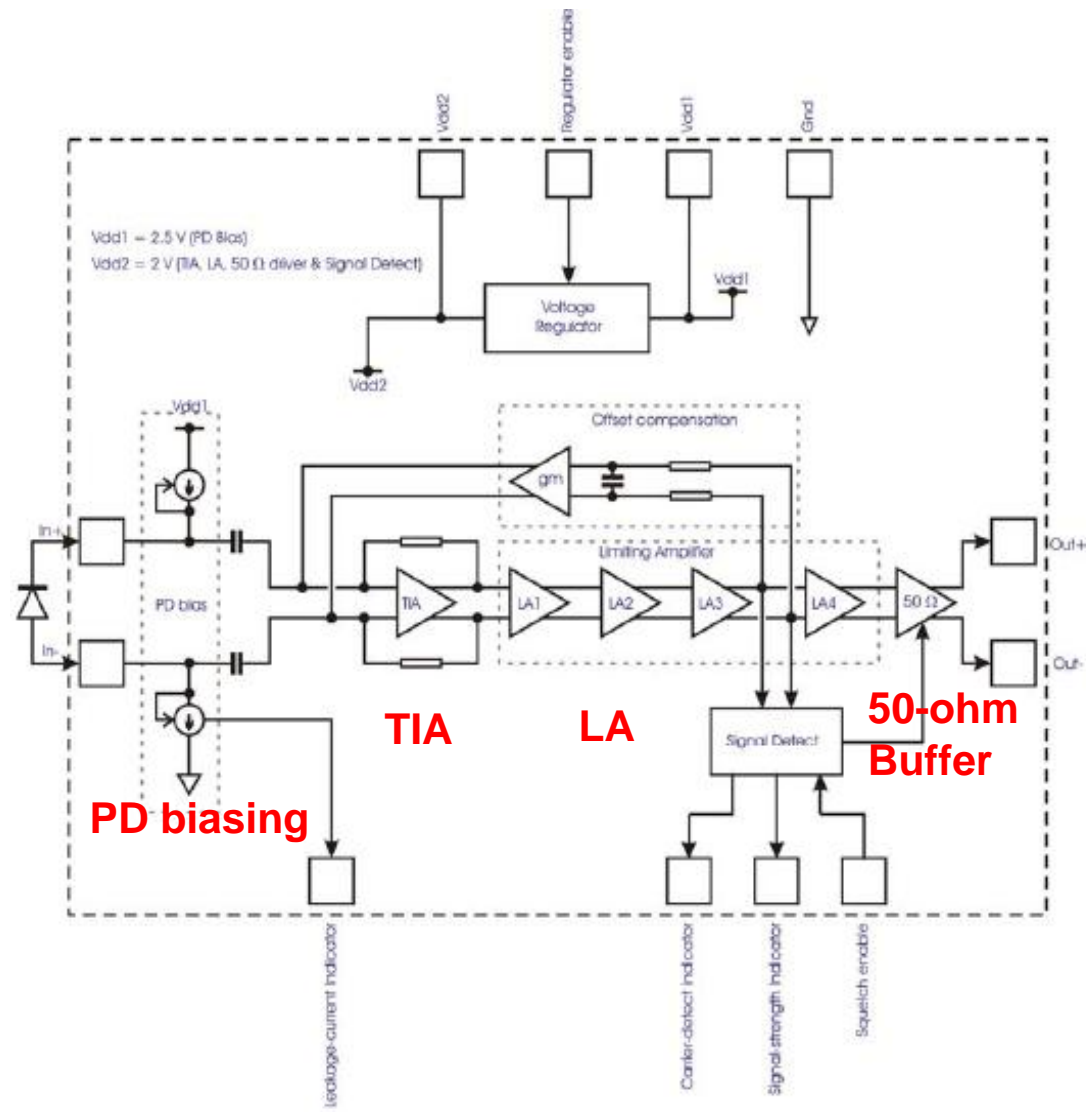
# A 5 Gbit/s Radiation-hard Optical Receiver for GBT

- ◆ A single chip consisting of
  - ◆ A Transimpedance amplifier
  - ◆ A Limiting amplifier
  - ◆ A 50  $\Omega$  line driver
- ◆ Main specifications:
  - ◆ Bit rate: 5 Gb/s (min)
  - ◆ Sensitivity: 20  $\mu$ A p-p ( $10^{-12}$  BER)
  - ◆ Total jitter: < 40 ps P-P
  - ◆ Dark current: 0 to 1 mA
  - ◆ Power supply : 2.5V  $\pm$  10%
  - ◆ Power consumption < 250 mW
  - ◆ Die size: 0.75 mm  $\times$  1.25 mm
  - ◆ Pin diode capacitance  $C_d \sim 400$  fF
  - ◆ Large range of temperature : From -20 C to 80 C
  - ◆ Radiation tolerant (up to 200 Mrad)
- ◆ Additional features :
  - ◆ Internal voltage regulator (with enable/disable control)
  - ◆ Leakage-current magnitude indicator
  - ◆ Squelch function (with enable/disable control)




# Overview of GBT Optical Receiver Design

- ◆ A fully differential architecture
  - ◆ Good power supply noise and common-mode noise rejection (PSRR and CMRR)
  - ◆ Minimize the effects of cross talk between the TIA and LA stages
  - ◆ On-chip AC coupling between the PD and TIA
- ◆ Transimpedance amplifier (TIA)
  - ◆ Define the sensitivity of the optical receiver-- low noise
  - ◆ High bandwidth, and high gain
  - ◆ Biasing and leakage current compensation for the PD
- ◆ Limiting Amplifier and output buffer (LA)
  - ◆ High gain and large output swing
  - ◆ Wide bandwidth
  - ◆ Offset level compensation
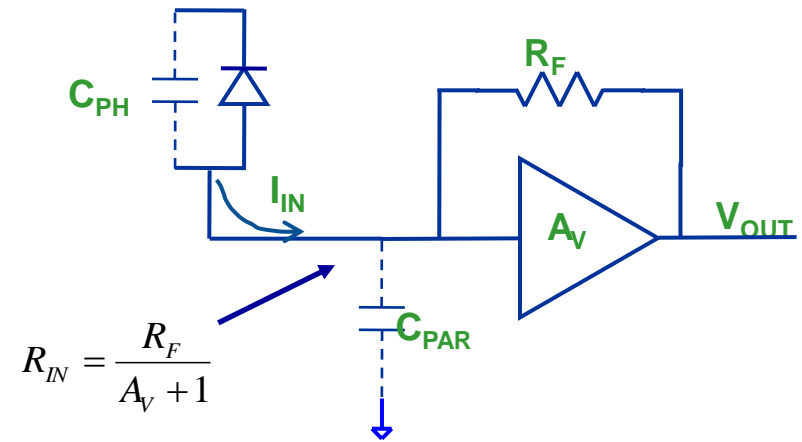
# Transimpedance Amplifier

- ◆ Shunt (resistive) feedback amplifier is widely used for high speed receiver designs
- ◆ To increase the bandwidth:
  - Lowering the  $R_f$
  - Increasing the amplifier open loop gain
  - Lowering the input node capacitance
- ◆ The noise contribution of the amplifier mainly comes from the input transistor
- ◆ To minimize this noise
  - Increasing the  $R_f$
  - Lowering the input node capacitance
  - Increasing the amplifier transconductance
- ◆ Large  $R_f$  for low noise and high transimpedance gain
- ◆  $R$  and  $C$  limit the bandwidth
- ◆ Techniques to extend the bandwidth



$$R_{IN} = \frac{R_F}{A_V + 1}$$

$$C_T = C_{PH} + C_{PAR} + C_{IN}$$


$$Z_T = \frac{v_{out}}{i_{in}} = \frac{-A_V}{A_V + 1} \frac{R_F}{1 + j\omega C_T \frac{R_F}{1 + A_V}}$$

$$BW = \frac{1 + |A_V|}{2\pi \cdot R_F C_T}$$


$$i_{n,in}^2 = \frac{4kT}{R_F} + \frac{4kT\Gamma}{R_F^2} \left( \frac{1}{g_m} + \frac{(2\pi \cdot f \cdot R_F C_T)^2}{g_m} \right)$$
 
# Bandwidth Extension Technique

- Inductive(shunt) peaking
  - Introduction of an inductor in series to resonant with the C, enhancing the bandwidth
  - The frequency response of this inductive peaking amplifier is characterized by the ratio  $m$
- $m=L/(R^2C)$




Factor $m$	Normalized $f_{3dB}$	Response
0	1.00	No shunt peaking
0.32	1.60	Optimum group delay
0.41	1.72	Maximally flat
0.71	1.85	Maximum bandwidth

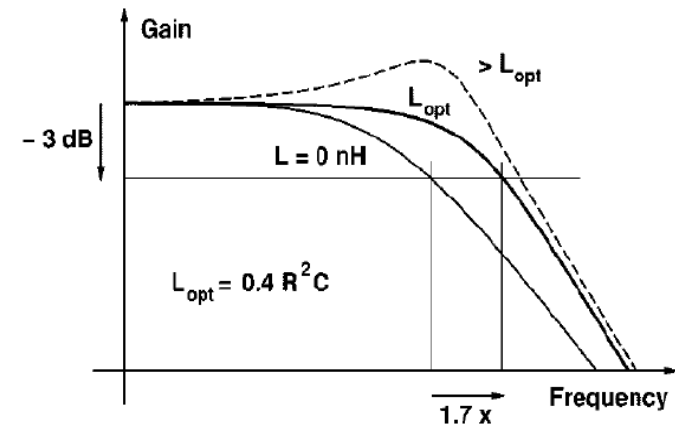





# GBT Transimpedance Amplifier

 

- ◆ Fully differential to minimize
  - cross talk
  - power supply noise
  - common-mode noise
- ◆ Inductive peaking
  - Extends the bandwidth
- ◆ Large input transistor for low noise
- ◆ Cascode
  - Reduces the Miller effect
- ◆ Drawback:
  - 2V supply required

	<i>SS, 100 °C</i>	<i>TT, 27 °C</i>	<i>FF, -20 °C</i>
<i>Gain</i>	<b>704 Ω</b>	<b>700 Ω</b>	<b>694 Ω</b>
<i>BW</i>	<b>4.0 GHz</b>	<b>5.1 GHz</b>	<b>6.0 GHz</b>
<i>Noise</i>	<b>3.4 μA</b>	<b>1.9 μA</b>	<b>10 μA</b>
<i>Power Dissipation</i>	<b><math>V_{dd} = 2.5V, I_{dd} = 14 mA, P = 35 mW</math></b>		


# GBT Limiting Amplifier

 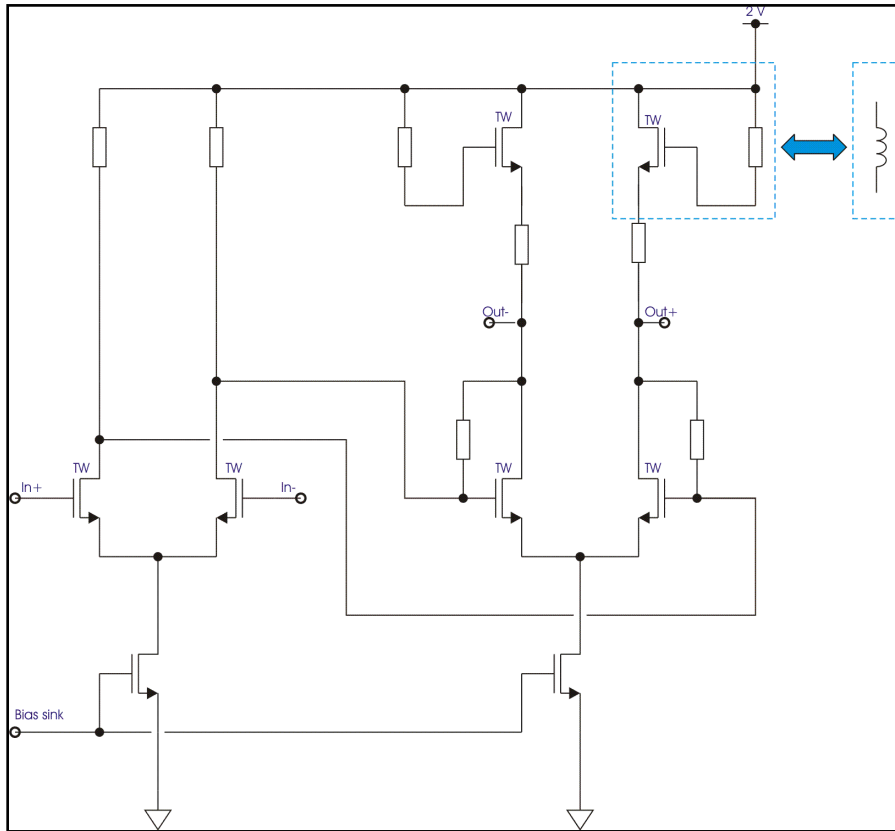


- ◆ **Modified Cherry and Hopper with resistive loading for high bandwidth**
- ◆ **Active inductive peaking**
  - **BW is increased by 34% by active inductive peaking**
- ◆ **Four gain stages**
  - **Four gain stages are used to keep the power from being too high.**
  - **Stages with increasingly larger driving strength to drive the 50-ohm output stage with high bandwidth.**
  - **“High gain” first stage to reduce the noise contribution from the following stages.**

	<i>SS, 100 °C</i>	<i>TT, 27 °C</i>	<i>FF, -20 °C</i>
<b>Gain</b>	<b>24</b>	<b>100</b>	<b>236</b>
<b>BW</b>	<b>4.0 GHz</b>	<b>4.5 GHz</b>	<b>5.0 GHz</b>
<b>Noise</b>	<b>200 <math>\mu</math>V</b>	<b>309 <math>\mu</math>V</b>	<b>465 <math>\mu</math>V</b>
<b>Power Dissipation</b>	<b><math>V_{dd} = 2.5 \text{ V}, I_{dd} = 24 \text{ mA}, P = 60 \text{ mW}</math></b>		

 
# Optical Receiver Chip Layout, Photograph, and Test Setup



 - ◆ Chip layout, implemented using 0.13  $\mu\text{m}$  IBM CMOS Process
- ◆ Die size 0.75 mm x 1.25 mm




◆ Chip microphotograph

 


◆ Chip along with the PD on testboard
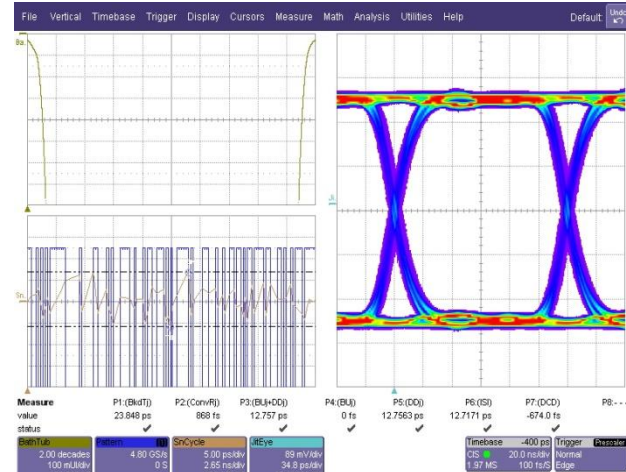
# Eye Diagram Measurements

- Measured differential eye diagrams at 5 Gbit/s for different optical power at the input (-6 dBm and -18 dBm)
  - Well opened eye diagram for -6 dBm and still correct at -18 dBm
  - The test PRBS sequence length is  $2^7-1$
  - A constant output swing of 400 mV
- For -6 dBm input :
  - Rise time = 30 ps
  - Total jitter = 0.15 UI @ BER =  $10^{-12}$  (UI = 200 ps)
- For -18 dBm input :
  - Rise time = 60 ps
  - Total jitter = 0.55 UI @ BER =  $10^{-12}$



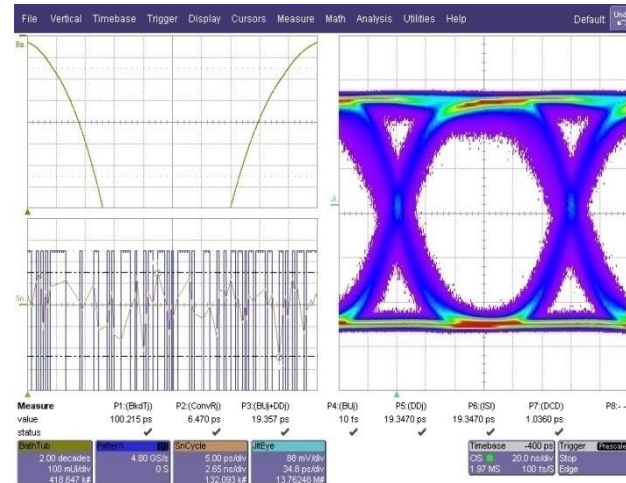
Eye diagram 5 Gbit/s optical power = -6 dBm




Eye diagram 5 Gbit/s optical power = -18 dBm




# Eye diagrams versus the Total Dose

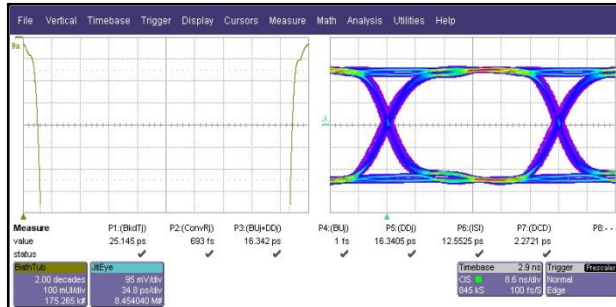


Pre-rad eye diagram (input=500 mV)

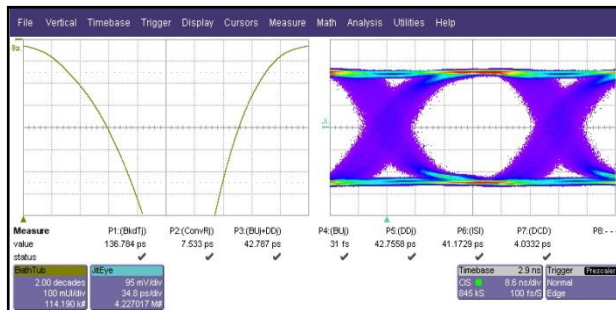

Pre-rad eye diagram (input=50 mV)

 

200 Mrad eye diagram (input=500 mV)

 


200 Mrad eye diagram (input=50 mV)


- ◆ Electrical board used for irradiation test
- ◆ Irradiation test done at CERN Xray facility 4 Mrad/hour
- ◆ Only the GBTIA chip is exposed to Xray beam
- ◆ No degradation is observed after a dose rate of 200 Mrad

# Bit Error Rate Measurements

## BER v.s. Input Optical Level

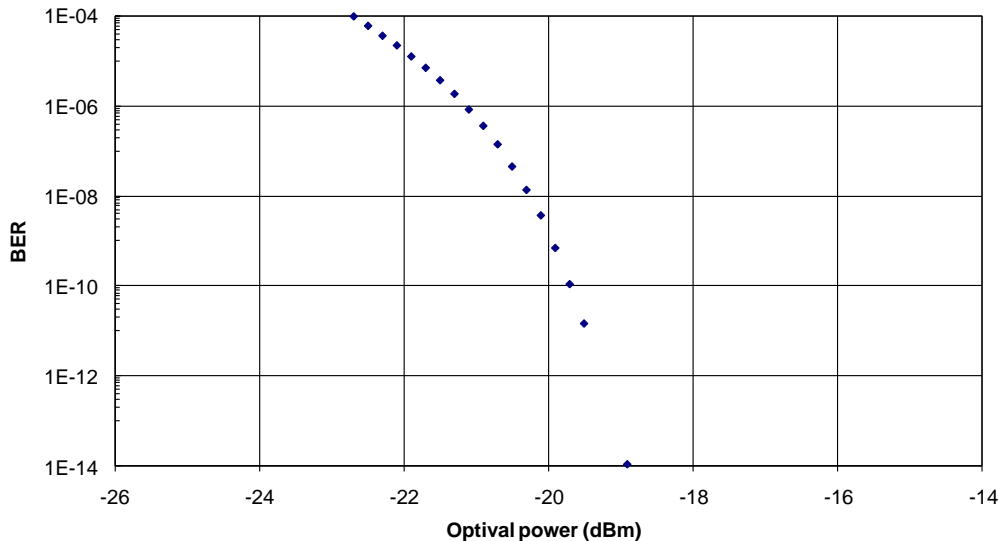

## BER v.s. Total Dose

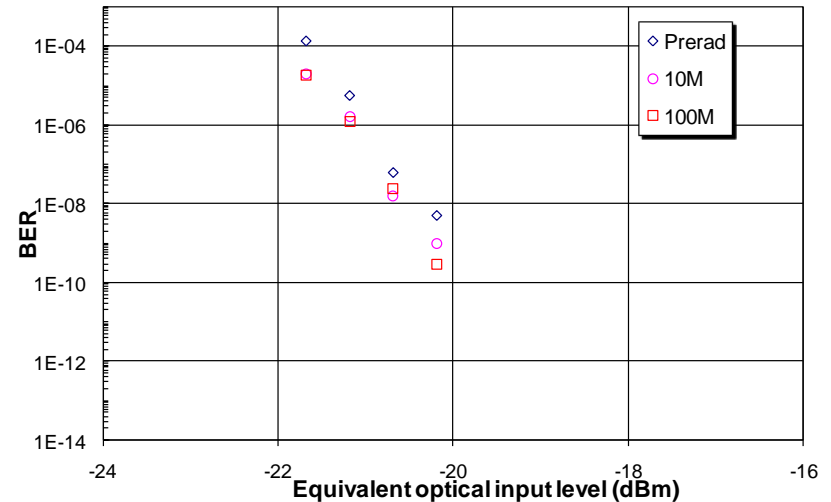

- ◆ For  $V_{dd}=2V$  and  $T=25\text{ }^{\circ}C$
- ◆ Data pattern : PRBS7
- ◆ The sensitivity for a BER of  $10^{-12}$  is estimated to be better than -19 dBm


- ◆ Effects of total dose (as high as 100MRad) is negligible.

# Performance Summary of the GBT Optical Receiver

- ◆ **Main Specifications in term of bandwidth and sensitivity are respected**
  - Eye diagram is well opened at 5 Gbit/s
  - BER v.s. the input current shows a good sensitivity
- ◆ **The effect of the leakage current is estimated**
  - The sensitivity is degraded by 4 dB
  - The value of the high pass cut off frequency still compatibility with the data encoding used for the GBT
- ◆ **Radiation effects :**
  - TID tolerance is proven
  - We have to estimate the single event upset tolerance

Bit rate	5 Gbit/s
Transimpedance gain	40 k $\Omega$
Output voltage	$\pm 0.2$ V (50 $\Omega$ )
Sensitivity for BER =10 <sup>-12</sup>	-19 dBm
Supply voltage	2 V $\pm$ 10%
Power consumption	95 mW
Radiation tolerance	> 200 Mrad
Penalty for high dark current	4 dB

# Phase Shifter in the GBT

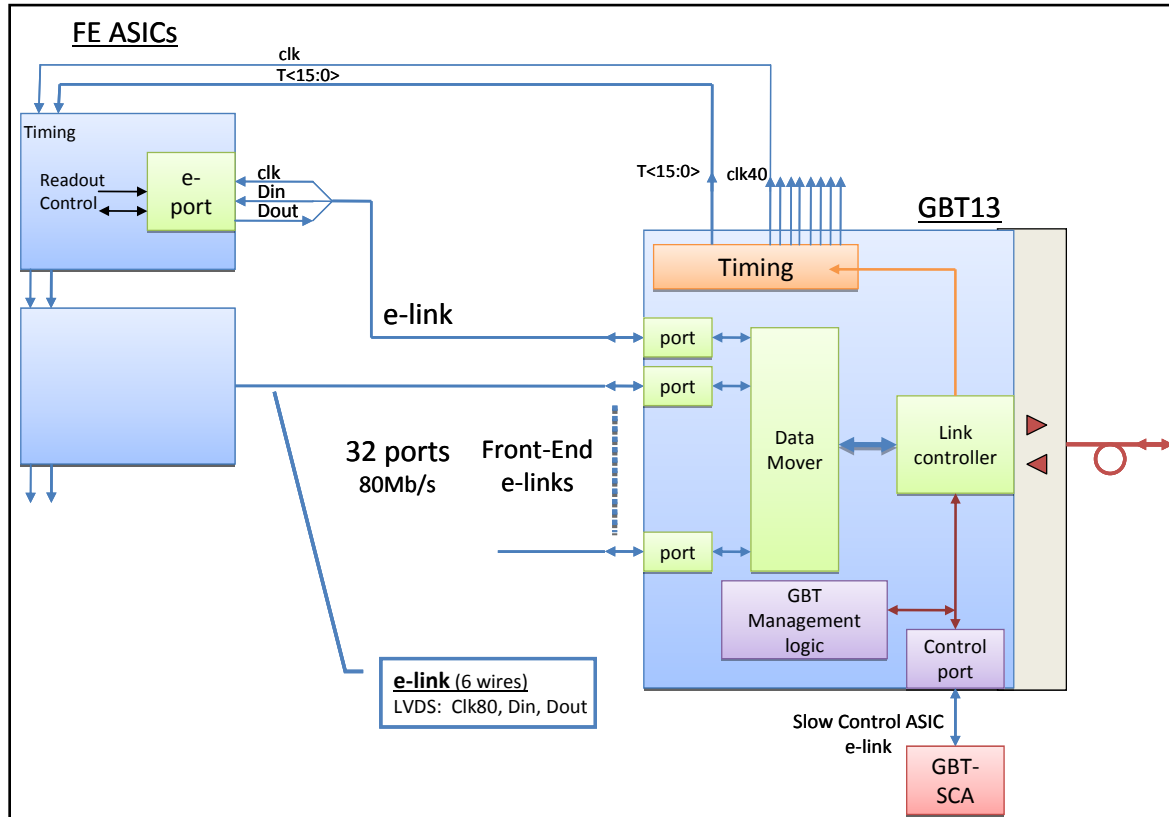


- ◆ To provide multiple (~8) clocks synchronized with the main clock for front-end ASICs with frequency of 40 MHz, 80 MHz, and 160 MHz.
- ◆ To allow for compensation of the cable/fiber lengths, the time-of-flight of particles and delays in the electronic circuits.
- ◆ The 8 reference clocks are programmable both in *phase* and *frequency*.
- ◆ The required phase resolution is *50 ps* independently of the clock frequency.



# Phase Shifter Specs


#	specification	min	typ	max	unit	note
	<b>Number of outputs</b>	<b>8</b>				
	<b>Frequencies</b>	<b>40, 80 and 160</b>			<b>MHz</b>	<b>programmable per output, set by control word Freq[1:0]</b>
	<b>Phase resolution</b>	<b>50</b>			<b>ps</b>	<b>Set by Delay[8:0]</b>
	<b>DNL</b>			<b>20%</b>	<b>LSB (50ps)</b>	
	<b>INL</b>			<b>30%</b>	<b>LSB (50ps)</b>	
	<b>Jitter RMS</b>			<b>5</b>	<b>ps</b>	
	<b>Jitter P-P</b>			<b>30</b>	<b>ps</b>	
	Temperature coefficient			5	ps/deg	
	Supply coefficient			50	ps/V	
	Logic levels					Programmable: CMOS/LVDS
	<b>Synchronized with the 40Mhz main clock</b>					

# Phase Shifter Architecture #1

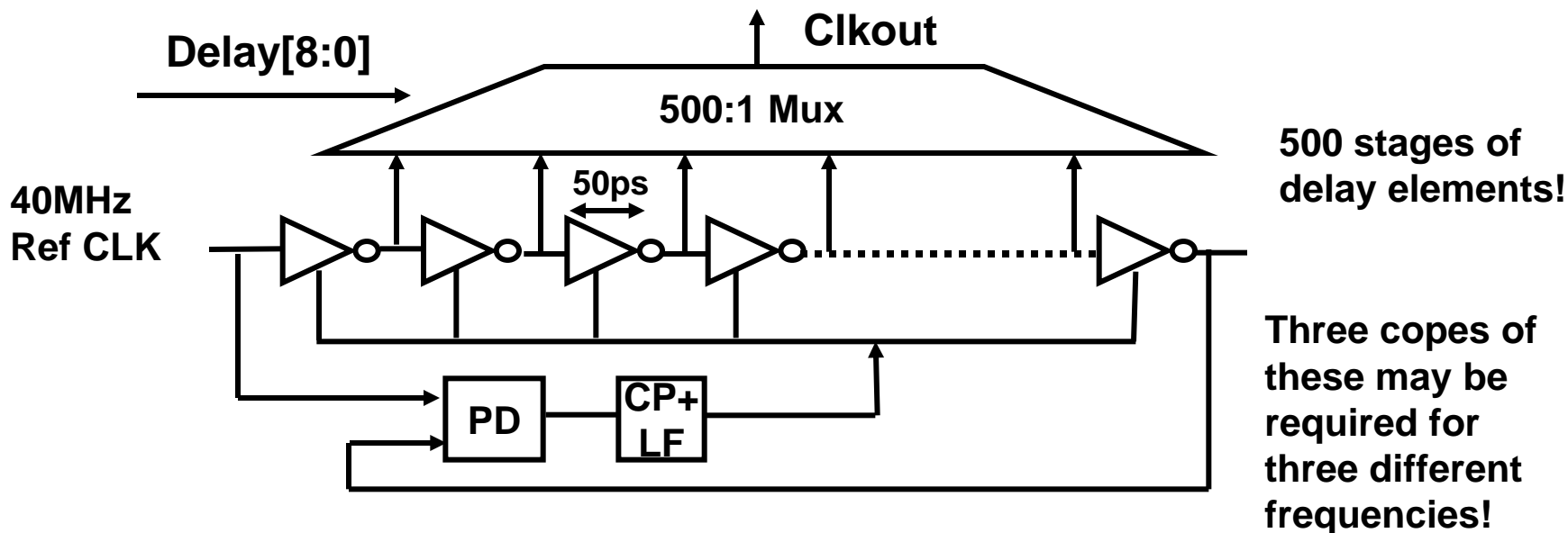

- ◆ 500 stages of delays are needed for a resolution of 50 ps in a range of 25 ns.
- ◆ Considerable amount of switching power and switching noise.


# Phase Shifter: Architecture #2

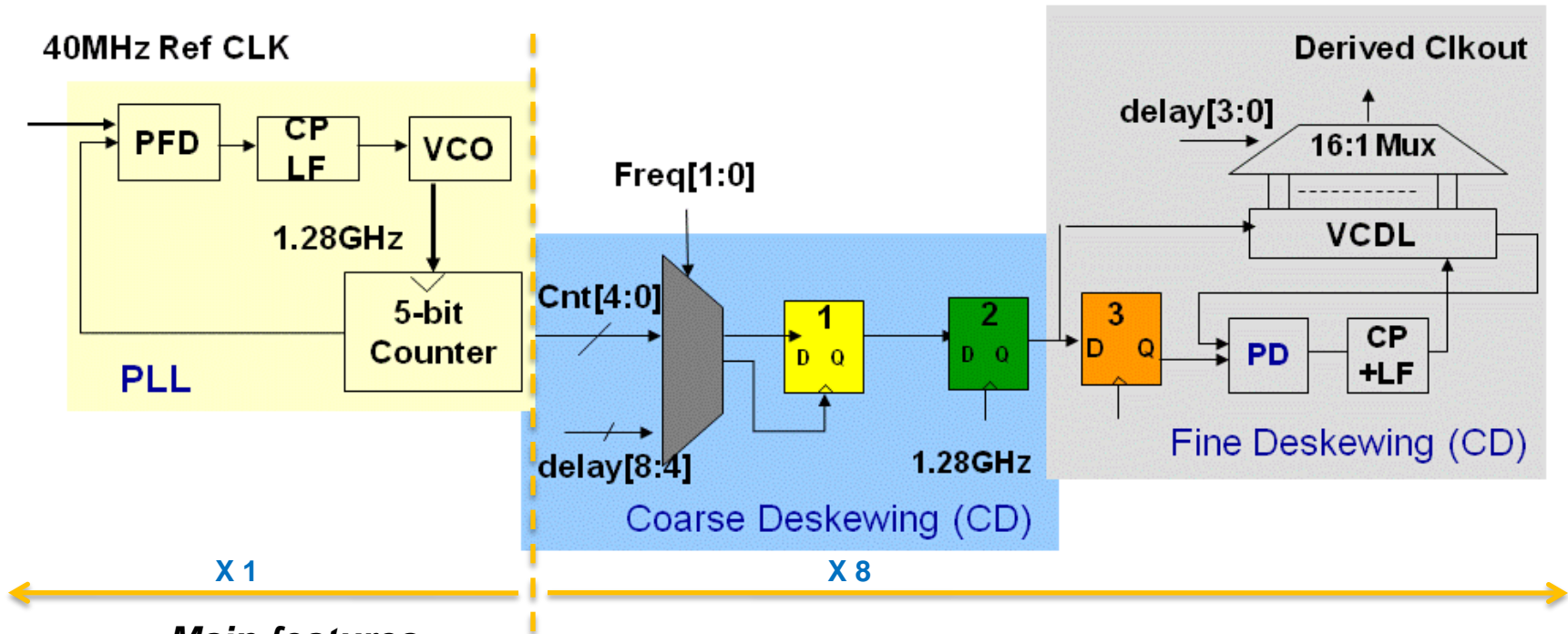

## Main features:

- 3 channels in the GBT – SerDes
- 1 PLL + Counter generates the three frequencies: 40 / 80 and 160 MHz
- 1 DLL per channel: 48.83 ps resolution
- Mixed digital/analogue phase shifting technique:
  - Coarse deskewing – Digital:  $\Delta t(\text{coarse}) = 781.25 \text{ ps}$
  - Fine deskewing – Analogue:  $\Delta t(\text{fine}) = 48.83 \text{ ps}$
- Power consumption: 5.6 mW/channel (simulated)
- Simulated Differential non-linearity: <6.7% LSB
- Simulated Integral non-linearity: INL<6.5% LSB


# GBT-SerDes Chip Layout

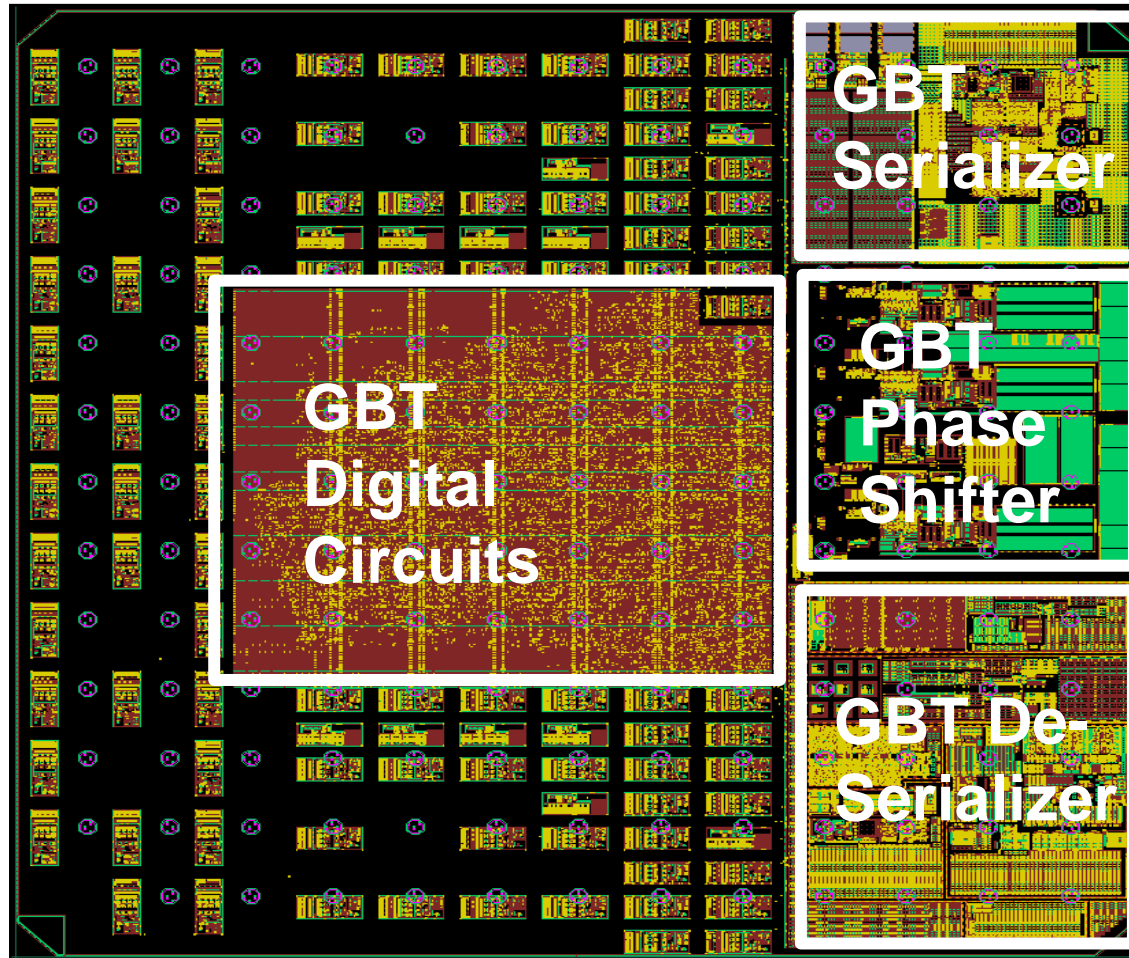

Packaged in a custom 13 × 13 bump-pad C4 package (168 pin)



# Test Setup

 

# Phase Shifter: Measurements

Resolution:  $\Delta t = 50$  ps

Differential Non-Linearity

$\sigma = 4.7$  ps (9.6% of  $\Delta t$ )



pp = 21.5 ps (44% of  $\Delta t$ )

Jitter:  $\sigma = 5$  ps (pp = 30 ps)

Integral Non-Linearity

$\sigma = 4.3$  ps (8.7% of  $\Delta t$ )

pp = 21.9 ps (48.7% of  $\Delta t$ )

  


# Transmitter Driver

- ◆ **Must interface to the receiver**
  - Signal swing
  - Common mode
  - AC couple (baseline wander)
- ◆ **Best signal integrity for the least amount of power**
  - Double termination to reduce reflections?
  - Drive strength? Pre emphasis?
- ◆ **Current Mode Logic (CML) v.s. Single-ended Dynamic-Logic such as Truly-Single-Phase-Clock (TSPC)**

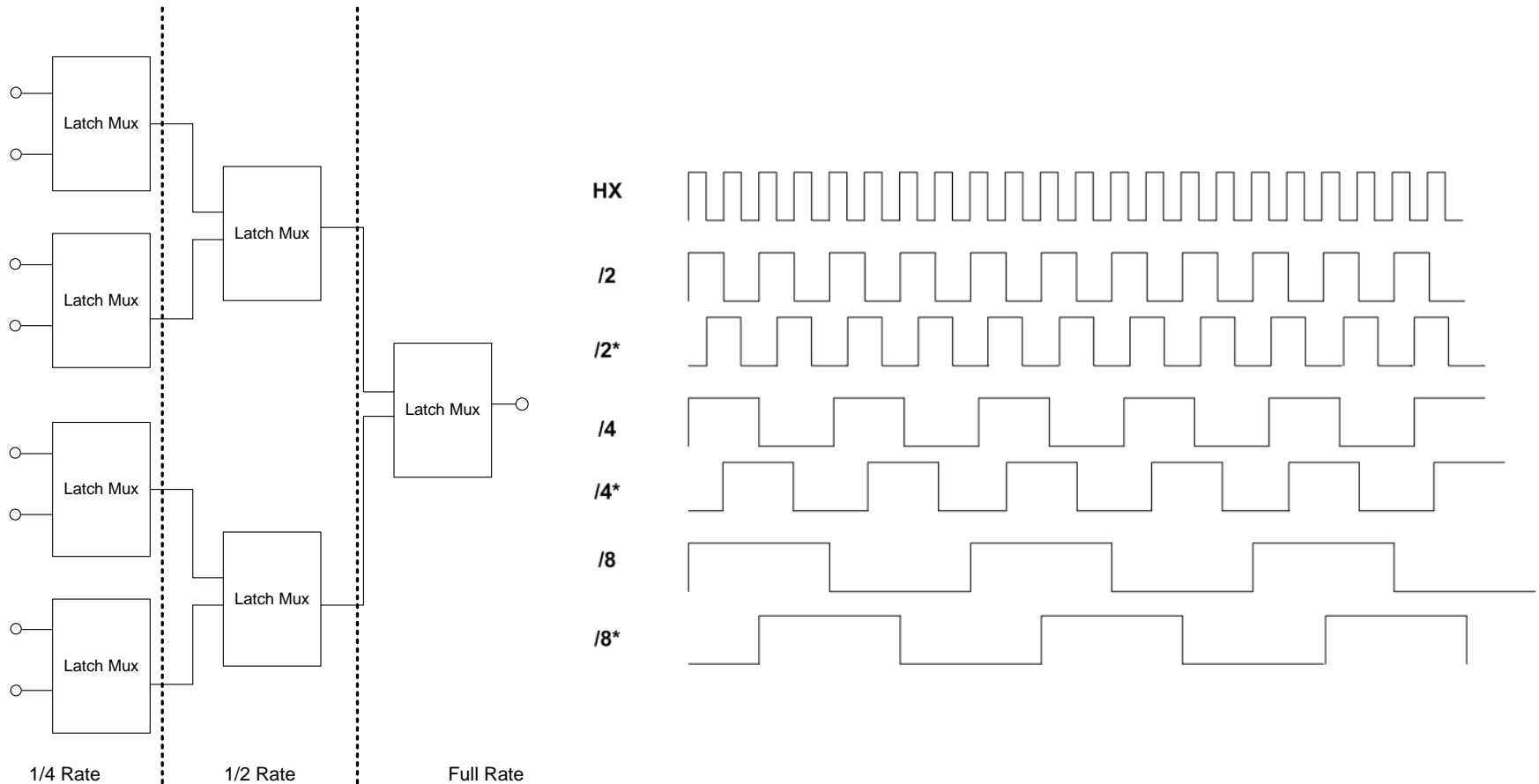
# Dynamic-Logic Serializer and Driver

- ◆ Dynamic CMOS gates (TSPC), no CML logic.
- ◆ “Christmas Tree” architecture (recursive).
- ◆ Poly phase clocking maximizes timing margin (speed).





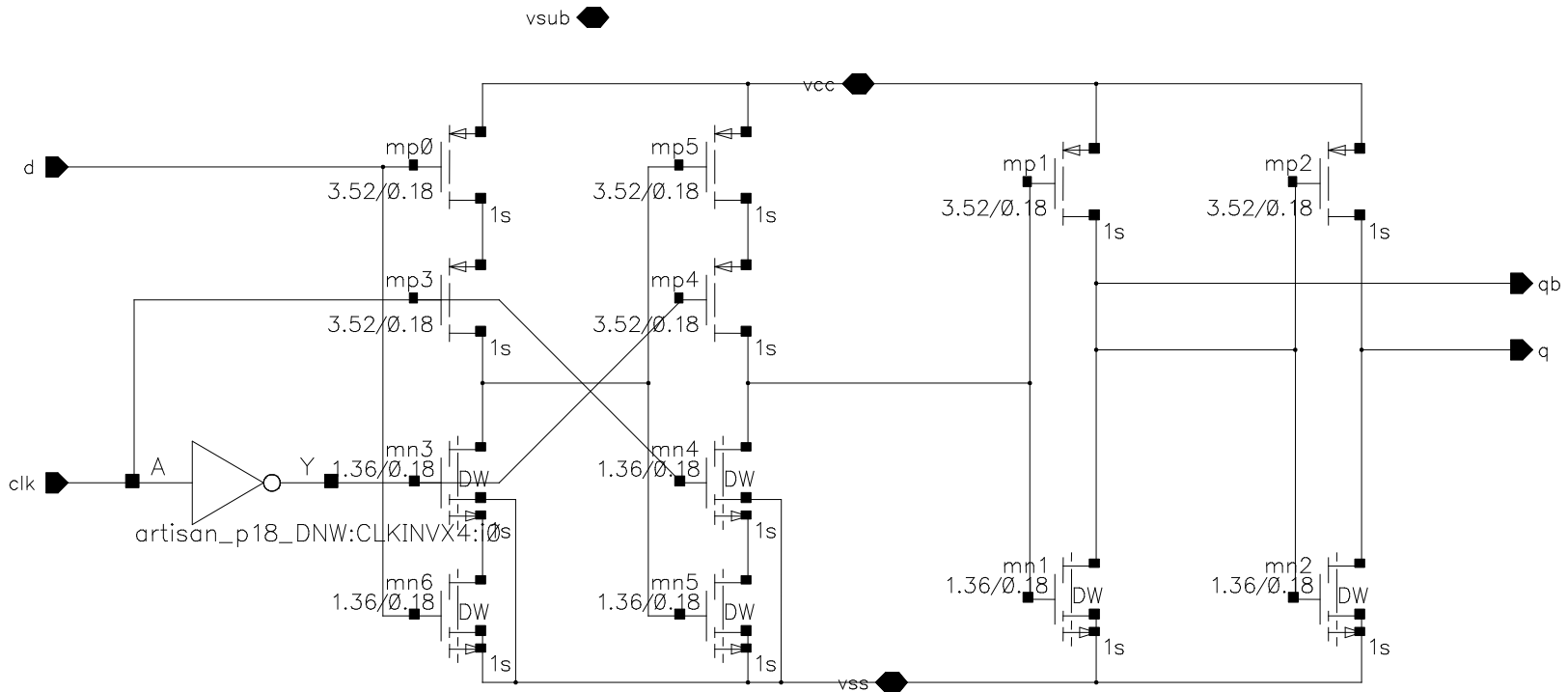
# Dynamic CMOS – TSPC (Truly Single Phase Clock)



 
# Push-Pull CML Driver for TSPC Serializer




- ◆ Push-Pull Operation, Lower power consumption compared to CML
- ◆ Differential swing is  $\pm I_{DD}R$ , where  $R=50\Omega$
- ◆ Bandwidth is  $1/(RC)$
 
# Dynamic-Logic Serializer and Driver Layout




<b>Serializer, Driver, and Pre-Driver</b>	
<b>Power @ 250MSPS (2G high speed clock)</b>	<b>34 mW</b>
<b>Area</b>	<b>400 <math>\mu\text{m}</math> x 160 <math>\mu\text{m}</math></b>

# Eye Diagram of 4Gbps 0.5inch FR4

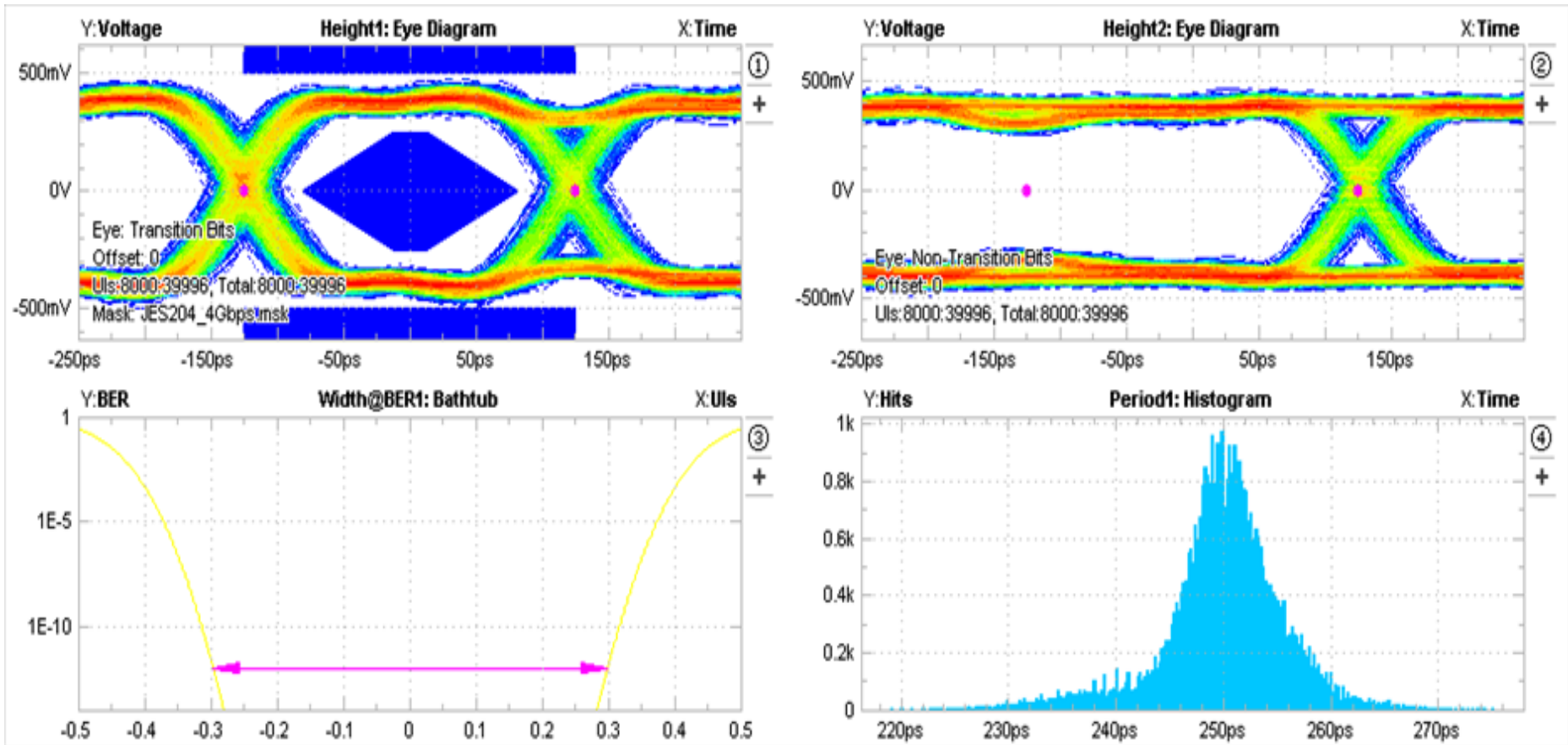


# CML Serializer and Driver

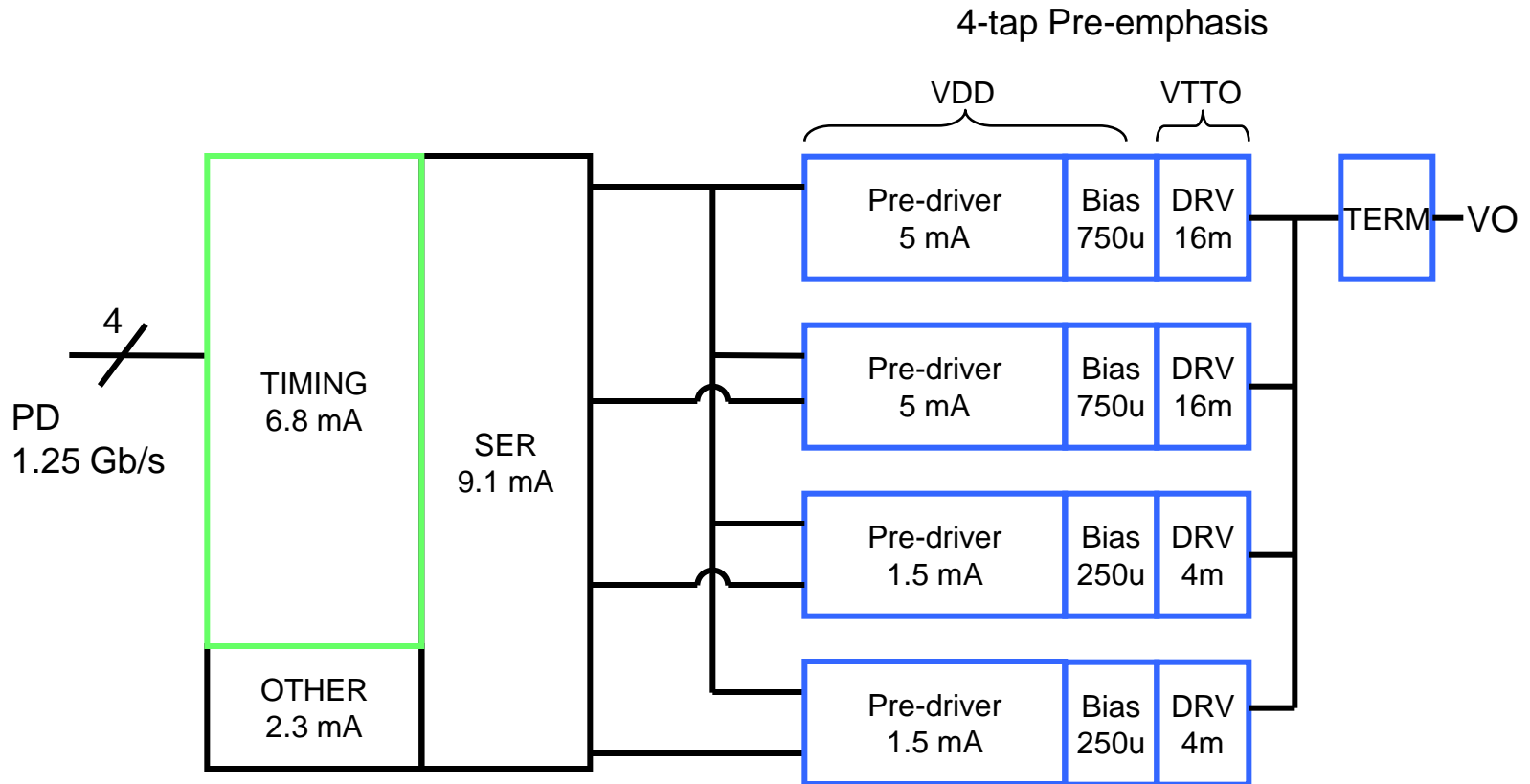

Synchronous TX (excluding serializer, etc.)	Power	Power (No PE)
Timing: bit alignment, sign swaps, etc.	12.2 mW	4.1 mW
Driver power (VDD)	27.0 mW	10.3 mW
Output power (max DC, max PE) (VTTO) (40mA max)	72.0 mW	25.6 mW
<b>Total</b>	<b>109.2mW</b>	<b>40 mW</b>

 
# CML Driver

$$I_{DD} = 16\text{mA}$$
$$P_{\text{STATIC}} = 28.8\text{mW}$$



- ◆ Resistive Internal termination absorbs reflections.
- ◆ High Power. Class A operation. Power dissipated in internal termination wasted.
- ◆ Differential swing is  $\pm 0.5I_{DD}R$
- ◆ Bandwidth is  $1/(2RC)$


# CML Serializer and Driver Layout

 

Synchronous TX (excluding serializer, etc.)	Area ( $\perp$ x $\parallel$ )
Timing Cell	$100\ \mu\text{m}$ x $140\ \mu\text{m}$
Driver (including inductors and pads)	<b><math>470\ \mu\text{m}</math> x <math>210\ \mu\text{m}</math></b>



# CML Transmitter (3Gbps 2.5inch FR4)


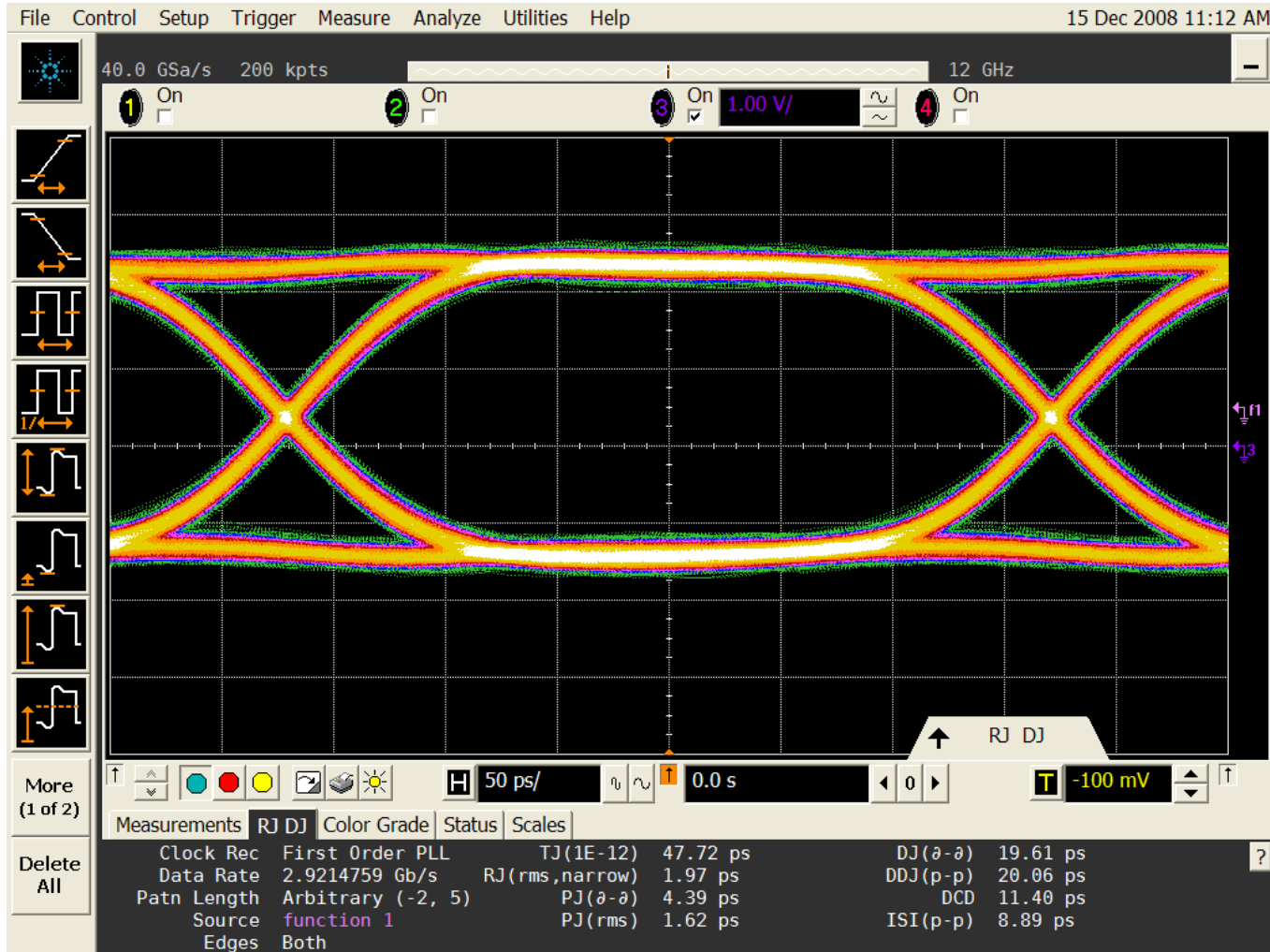


TJ = 48ps pp = 0.15UI pp

Fermi Lab, 10/05/2010




# Silicon-on-Sapphire CMOS Technology

  

- ◆ Insulating sapphire substrate
- ◆ A very thin silicon layer (100 nm)
- ◆ Reduced parasitic capacitance
  - Low power consumption
  - Minimum crosstalk
  - High integration of RF, mixed-signal, passive elements and digital functions on a single device.
- ◆ Optically transparent substrate
- ◆ Good immunity to SEEs
- ◆ Substrate is a good thermal conductor
- ◆ Sustaining low temperature
 
# Low Power CMOS OE Transceiver ICs in Silicon-on-Sapphire Technology




Performance:

4-channel  
optoelectronic  
transceiver  
0.6Gb/s

Innovation:

Dynamic adjust power at  
the transmitting side

DARPA OE-center

 


Performance:

4-channel  
optoelectronic  
transceiver  
2-3Gb/s

Innovation:

Instant power-up/down

DARPA PCA/RATS

 

Performance:

4-channel  
optoelectronic  
transceiver  
3-4Gb/s

Innovation:


Dual-rate  
(power-performance  
trade off)

DARPA C2OI

All using 0.5  $\mu\text{m}$  CMOS Silicon-on-Sapphire Technology


# Transceiver IC with OE Devices

## Optical Receiver ASIC

 


Detector chip attached

## VCSEL Driver ASIC


 


VCSEL chip attached

# VCSEL Driver Circuit

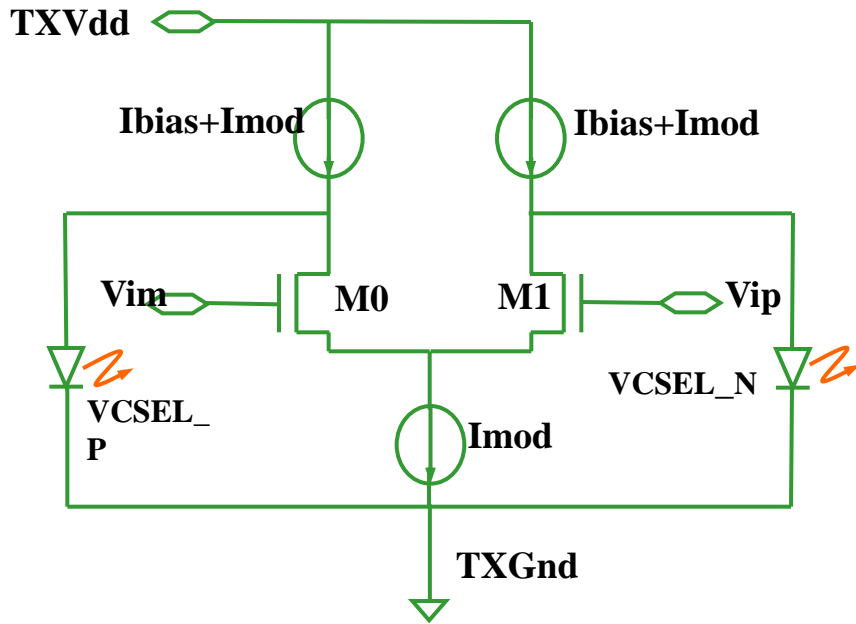



TX Bias(Modulation) current output

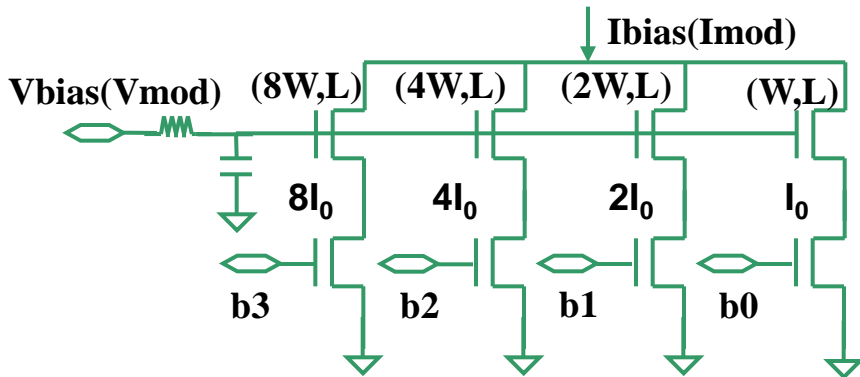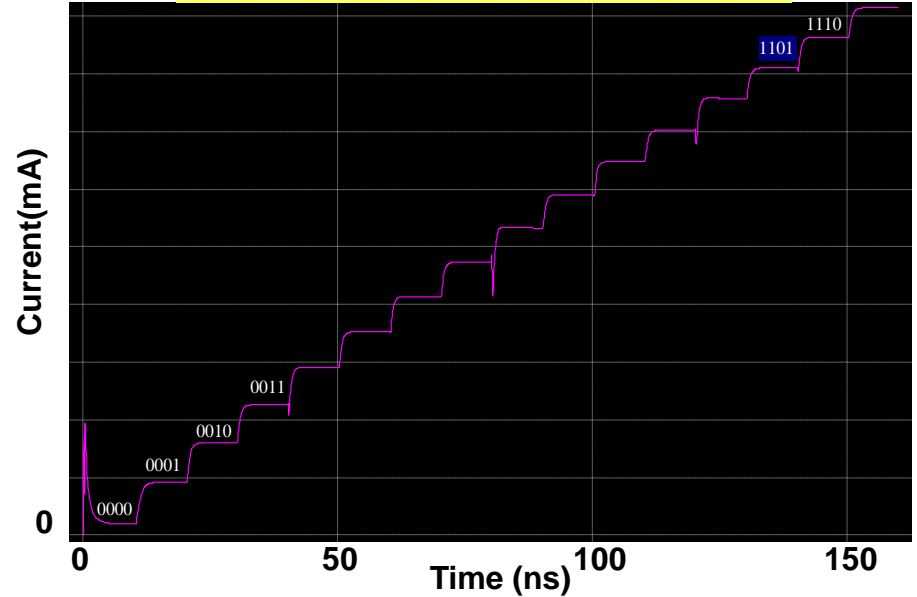


**DAC structure for Bias and Modulation Current**  
**b3 b2 b1 b0 are digital control bits**

**Digital-to-Analog Converter (DAC) structure allows adjustment of individual Ibias and Imod for greater flexibility.**

# Laser Driver Eye Diagram


 
 


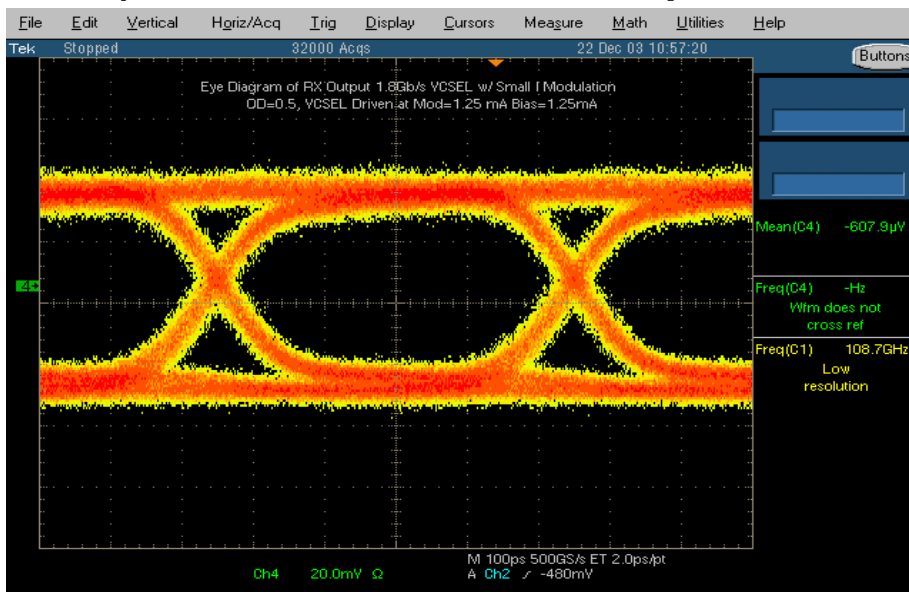( $2^{15}-1$  Pseudo random data pattern were used)



2.0 Gb/s
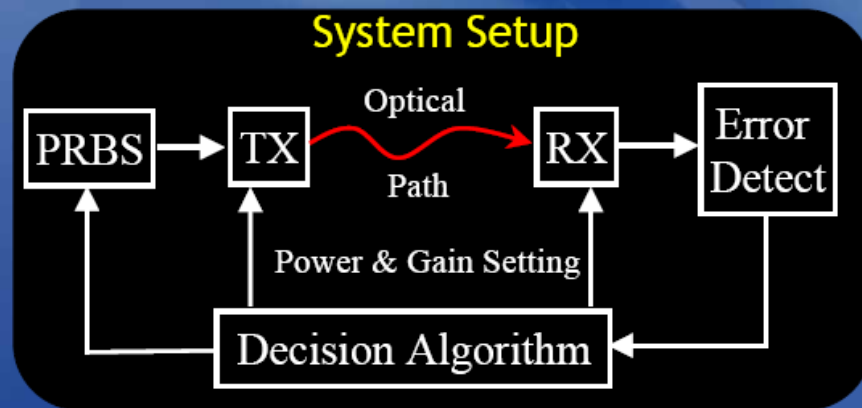  
# Dynamic Power Optimization Optical Link




Experiment to Find Optimum Power Setting for VCSEL Driver With and Without Optical Attenuation Filter for  $10^{-10}$  BER

	Receiver Gain Setting	Optimum Power Setting	
		Modulation Current (mA)	Bias current (mA)
Without Filter	Gmax	0.45	1.5
With Filter	Gmax	0.75	1.5






# Instant On/off optical link demonstration

2Gb/s Transmitter Eyes

 


2Gb/s Link (TX+RX) Eyes

   


*Complete power cycling (on/off) for a gigabit optical link demonstrated at 5-10nSec.*

# Dual Rate Optical Link

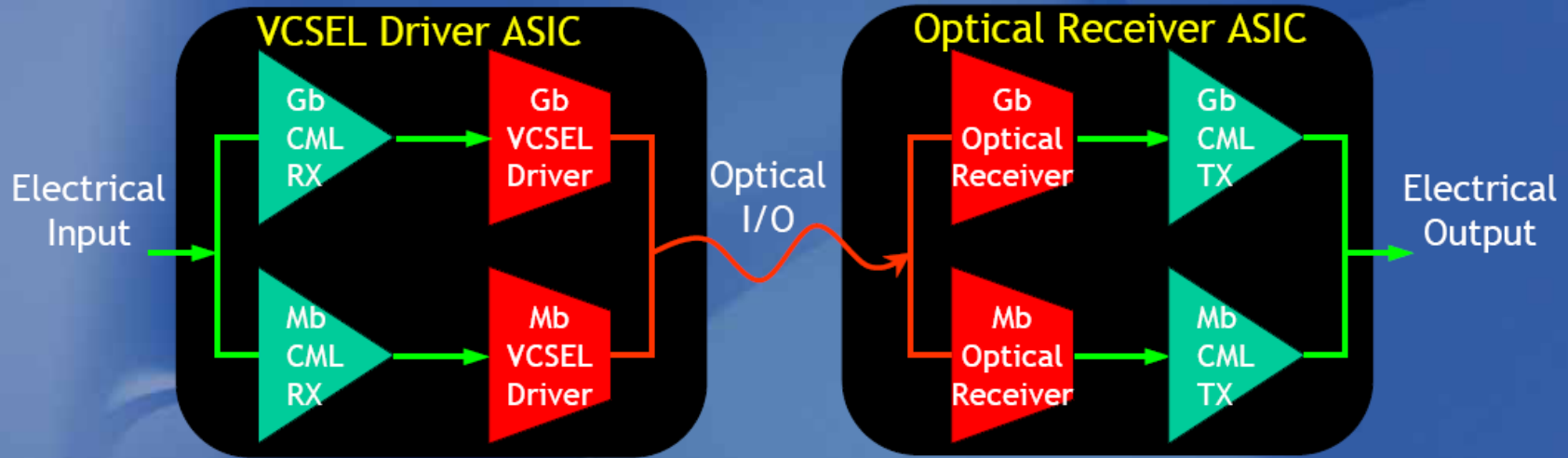


1.5Gb/s Link (TX/RX) Eye

 

104mW  
@ 1.5Gb/s


9mW @ 5Mb/s  
11X Reduction!!!

5Mb/s Link (TX/RX) Eye

 



 
# Low Phase Noise, 0.2 to 6 GHz Wideband LC Fractional-N PLL




- ◆ TSMC 0.13  $\mu\text{m}$  CMOS
- ◆ Frequency range: 0.2 to 6 GHz
- ◆ I and Q outputs
- ◆ Phase noise: -122 dBc/Hz @1MHz offset (2.4 GHz band)
- ◆ Reference spur: better than -69 dBc@40MHz
- ◆ Fractional spur: better than -73 dBc@1MHz
- ◆ Die area: 1.36 mm  $\times$  1.37mm
- ◆ Power: 35.6 ~ 52.62 mW
- ◆ Supports multi-band wireless communication standards including DCS1800, WCDMA, TD-SCDMA, Bluetooth, 802.11 a/b/g
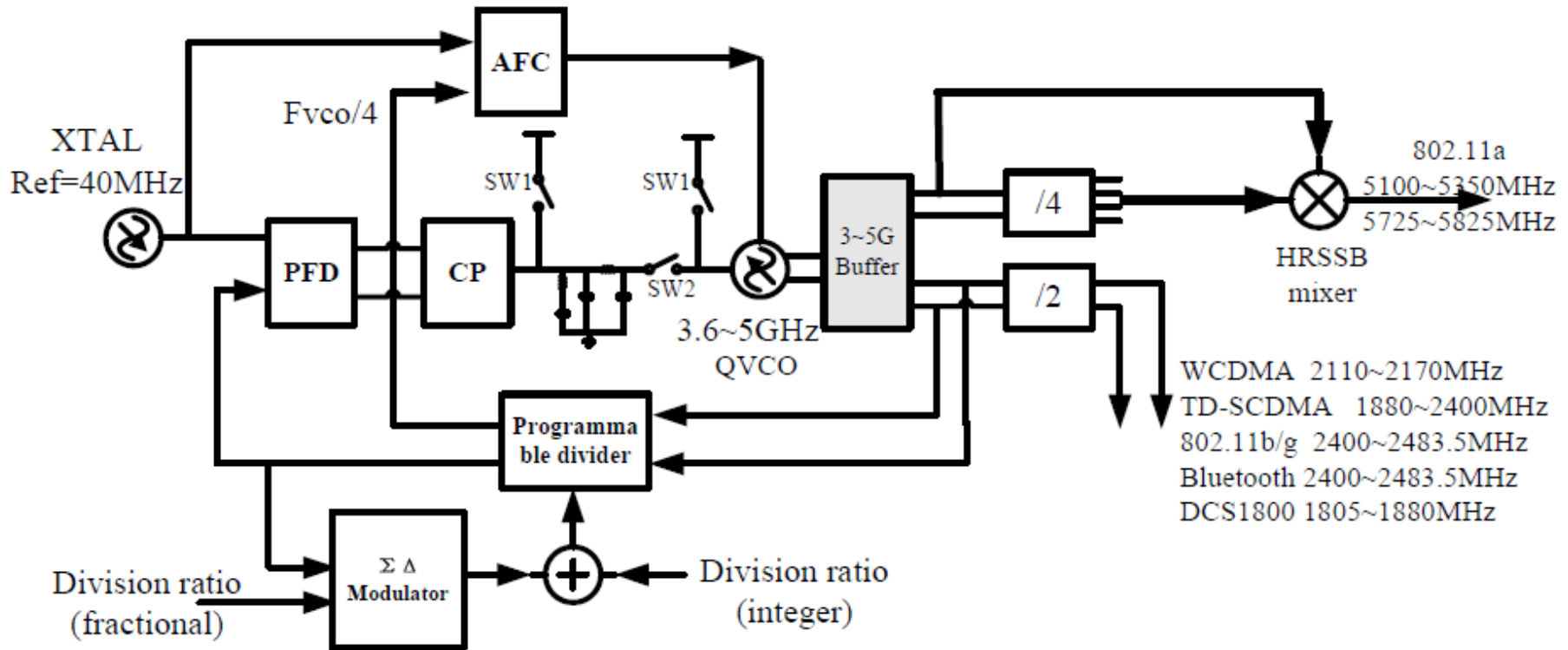
# Frequency Synthesizer Architecture

- ◆ QVCO with HR-SSB mixer
  - ◆ Two cross-coupled LC oscillator to provide I and Q
  - ◆ HR-SSB mixer is used to suppress spurs
  - ◆ High frequency VCO with divider is avoided by QVCO
  - ◆ Achieves both low power and lower-spur




# Measurement Results—Phase noise

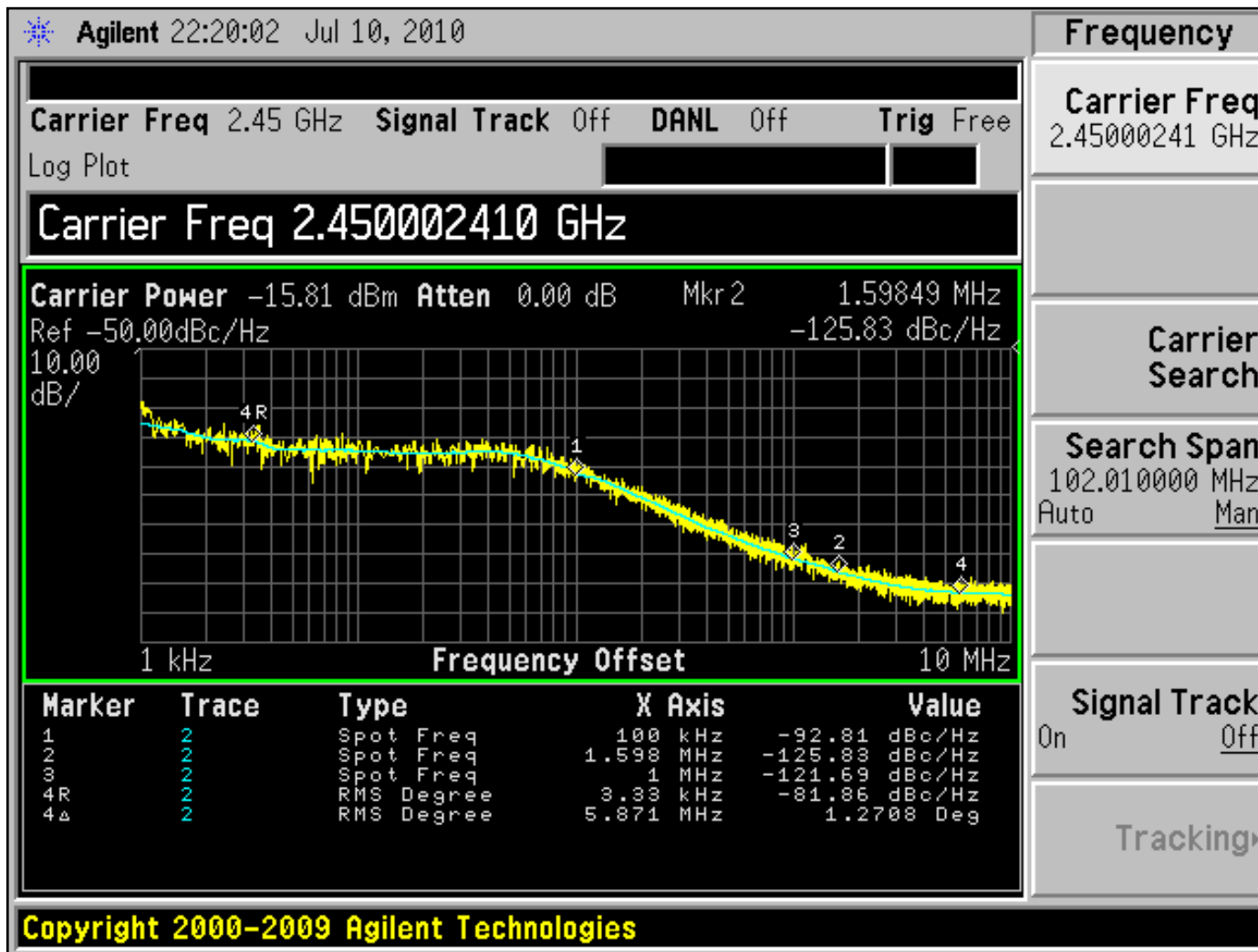

# Measurement Results Summary


Standards	Phase noise	RMS phase noise
<b>DCS1800</b> (1805~1880MHz)	-119.18dBc/Hz@600kHz -129.43dBc/Hz@1.6MHz -133.17dBc/Hz@3MHz	0.904°
<b>WCDMA</b> (2110~2170MHz)	-94.72dBc/Hz@100kHz -118.4dBc/Hz@600kHz -124.3dBc/Hz@1MHz	0.975°
<b>TD-SCDMA</b> (1880~2400MHz)	-93.46dBc/Hz@100kHz -122.55dBc/Hz@1MHz -126.29dBc/Hz@1.6MHz	1.789°
<b>Bluetooth</b> (2400~2480MHz)	-92.81dBc/Hz@100kHz -121.69dBc/Hz@1MHz -125.83dBc/Hz@1.6MHz	1.267°
<b>802.11b/g</b> (2400~2480MHz)	-92.81dBc/Hz@100kHz -121.69dBc/Hz@1MHz -125.83dBc/Hz@1.6MHz	1.267°
<b>802.11a</b> (5180~5805MHz)	-85dBc/Hz@100kHz -107.63dBc/Hz@600kHz -114.17dBc/Hz@1MHz	2.65°
<b>Loop bandwidth</b>	60 kHz ~ 90 kHz	
<b>Locking time</b>	<50 μs	
<b>Reference Spur</b>	<-69dBc@40MHz	
<b>Fractional Spur</b>	-72.93dBc@1MHz	
<b>Power</b>	35.6 ~ 52.62 mW	
<b>Die Area</b>	1.36×1.37mm <sup>2</sup> (core circuits)	

# Ring PLL

 

- ◆ 0.35 μm CMOS
- ◆ Area: 600 μm x 500 μm
- ◆ Power: 18 mW
- ◆ Frequency range: 400MHz to 2GHz
  - ◆ Support data-rate from 800 Mb/s to 4 Gb/s
- ◆ Jitter is less than 5 ps rms supporting BER of  $10^{-12}$ 
  - VCO phase noise: -92 dBc/Hz at 1MHz offset
  - VCO phase noise with bias circuit: -85 dBc/Hz at 1MHz offset
- ◆ CML outputs for efficient chip clock distribution

# Ring VCO Phase Noise

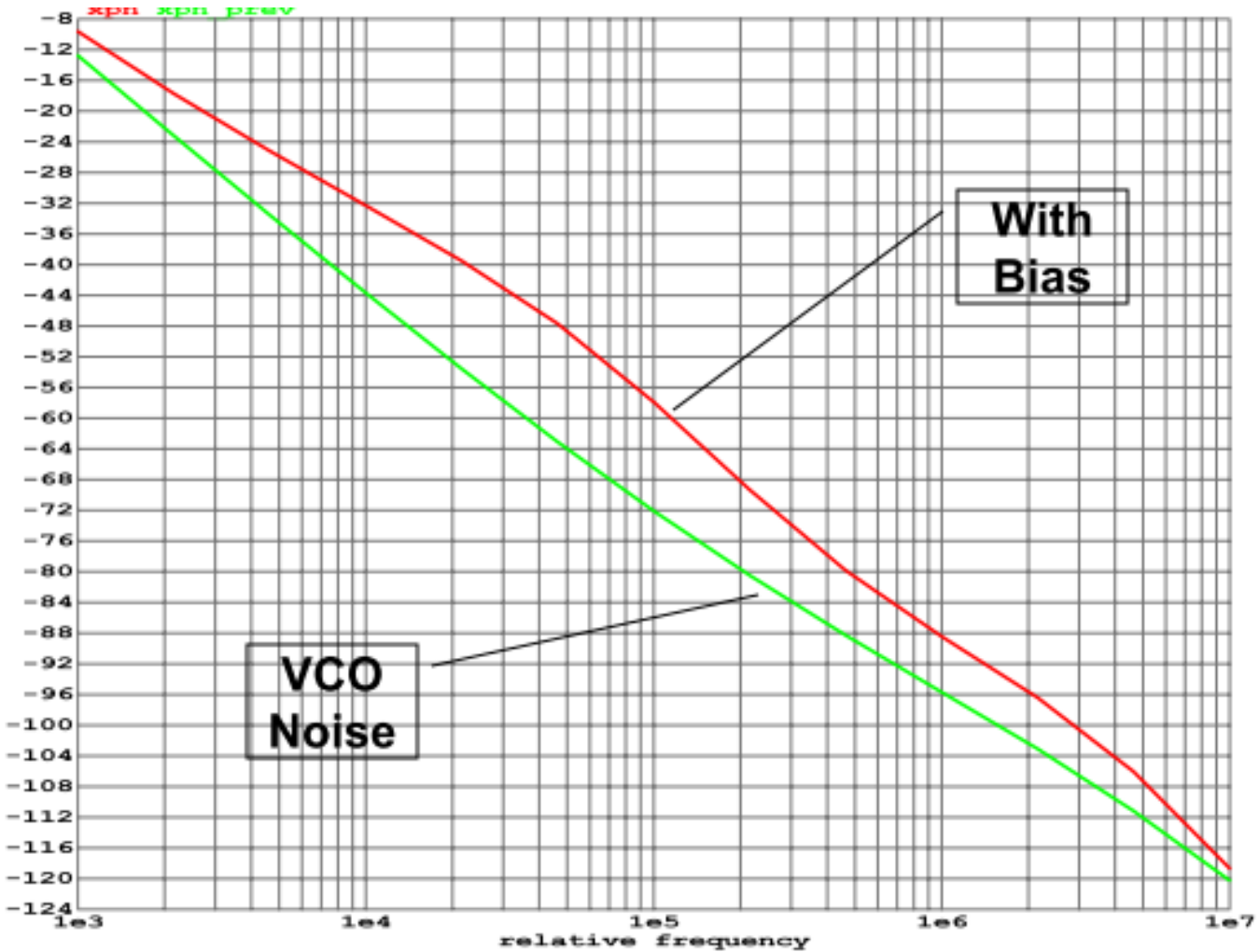

VCO phase noise: -92 dBc/Hz at 1MHz offset

# Summary

## ◆ Research Experience

### ● High-Speed Transmitter and Receiver

- ◆ Serializer, Line Driver and Laser Driver
- ◆ Radiation-Tolerant Optical Receiver

### ● Phase Locked Loops

- ◆ LC-Tank Based PLL
- ◆ Ring PLL

## ◆ Collaboration with Fermi Lab



# Q & A

◆ Thank You!